

11

Protected qubits using
Josephson junctions and other
superconducting elements.

Goal : all-electric protected*
qubits

Qubits are not elementary devices
(classical bits are not elementary
either: an implementation
consists of several transistors.)


Sub-goal : find a set of basic
elements for quantum
electric circuits

* Protected =

All unwanted interactions are
exponentially suppressed.

"Simple" elements:

Capacitor:

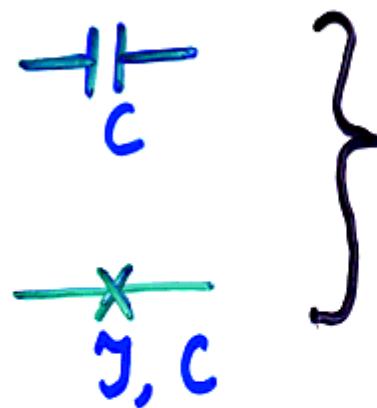

Standard

Josephson junction:



Inductor:




Usually implemented
as a chain of
Josephson junctions

$$J \gg \frac{e^2}{C}$$

$$(L_{\text{eff}} = N \left(\frac{\hbar}{2e} \right)^2 J^{-1})$$

Switch:

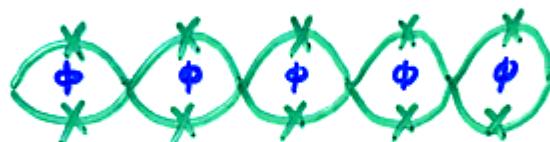

(Haviland et al)
2000

$$\phi \approx \pi$$

$$\Rightarrow$$


transition to
an insulating
state

(In dimensional
units, $\phi \approx \frac{\Phi_0}{2}$)

More exotic elements :

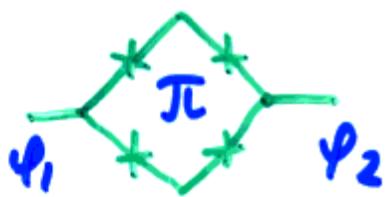
1) $0-\pi$ - contact

(Douçot, Vidal 2002
Ioffe, Feigelman 2002)



$$E = -J_1 \cos 2\varphi - J_2 \cos \varphi$$

$$J_2 \ll J_1, \quad \text{error term}$$

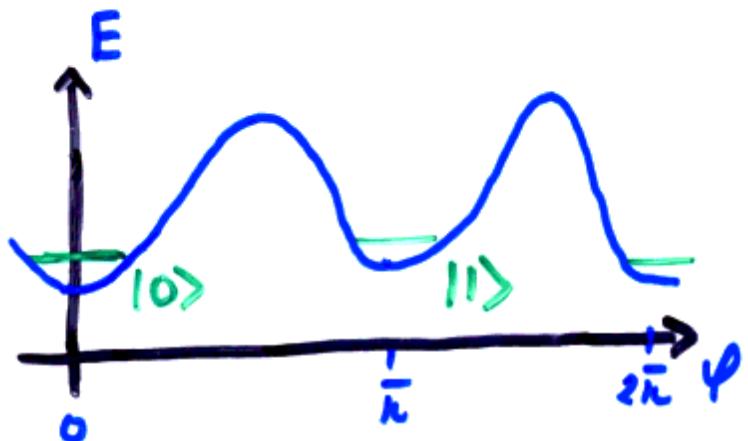


$$\delta E = E_1 - E_0 = 2J_2,$$

May depend on the environment \Rightarrow decoherence

2) Protection (stabilization)

$$\delta E_{\text{eff}} \rightarrow 0$$

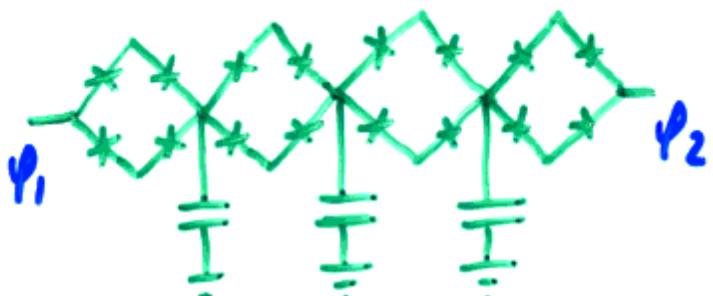

$$|0_L\rangle = |0000\rangle + |1100\rangle + \dots$$

(even number of 1s)

$$J_{1,\text{eff}} \sim \frac{1}{N}$$

$$\delta E_{\text{eff}} \sim \left(\frac{J_2}{t}\right)^{N-1}$$

tunneling amplitude

$$|1_L\rangle = |1000\rangle + |0100\rangle + \dots$$

(odd number of 1s)

It seems that quantum protection requires a many-body system because a protected state is similar to a quantum code.

Not quite true : One can use a single continuous degree of freedom for quantum encoding (Gottesman
Kitaev
Preskill 2000)

Main conceptual result of the present work :


A sufficiently large superconducting inductor provides room for quantum encoding.

(Of course, Josephson junctions are also needed)

Conventions: $\hbar = 1$, $2e = 1$.

Resistance unit: $\frac{\hbar}{(2e)^2} \approx 1 \text{ k}\Omega$

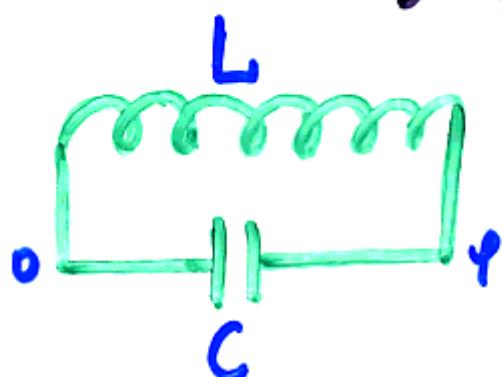In this units, the quantum resistance is simply $R_q = \frac{\hbar}{(2e)^2} \approx 6 \text{ k}\Omega$.



$$H = \frac{\Psi^2}{2L} + \frac{1}{2C} \underbrace{\left(i \frac{\partial \Psi}{\partial \varphi} \right)^2}_{q \text{ (charge operator)}}$$

$$\langle \Psi^2 \rangle = \frac{1}{2} \sqrt{\frac{L}{C}} \quad (\text{characteristic impedance})$$

"Superinductor": $\langle \Psi^2 \rangle$ is large,

$$\langle e^{i\varphi} \rangle = e^{-\frac{\langle \Psi^2 \rangle}{2}} = \exp\left(-\frac{1}{4} \sqrt{\frac{L}{C}}\right)$$

$$\sqrt{\frac{L}{C}} \gg 4 \quad (4 \text{ k}\Omega \text{ in the usual units})$$

in units of


$$\frac{\hbar}{2e^2}$$

How to make a superinductor?

1) Coil of n loops: $\sqrt{\frac{L}{C_{\text{geom}}}} \sim R_{\text{vac}} \sqrt{\frac{M}{\epsilon}} n$

$$R_{\text{vac}} = \frac{4\pi L}{137} \quad \left(\frac{4\pi}{c} \approx 377 \Omega \right)$$

Too many loops are needed

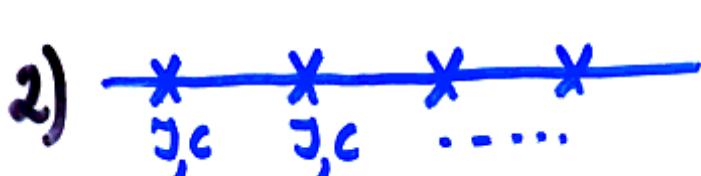2)  $L = \frac{N}{j}$

$\sqrt{\frac{L}{C_{\text{chain}}}} = \frac{N}{\sqrt{jC}} \gg 1$, but $\sqrt{jC} \gg 1$ is necessary to prevent phase slips.

Too many junctions...

3) Kinetic inductance

d 

(Amorphous film)

$$L = \frac{\ell}{d g_s} \sim \frac{\ell}{d} \frac{R_{\square}}{\pi \Delta}$$

normal state resistance $= \frac{R}{\pi \Delta}$

(Assuming that quantum fluctuations are not too strong)

7


For kinetic inductors, $C_{\text{geom.}}$ is not a limiting factor because usually $\frac{1}{\sqrt{LC_{\text{geom}}}} > \Delta$.

$$\langle \varphi^2 \rangle \sim R = \frac{l}{d} R_\square \quad \text{It is possible that } R_\square \sim 4 \text{ k}\Omega$$

Superinductor requirements:

- 1) $\frac{l}{d} \gg \frac{4}{R_\square}$
- 2) $d \gg \begin{cases} \text{to prevent phase slips} \\ \sim 30\text{\AA} \text{ in MoGe} \end{cases}$

Typical application:

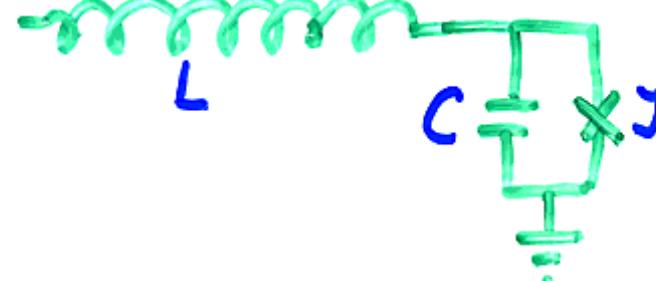


$$M = \sqrt{\gamma C} \sim 1 \quad (\text{intermediate quantum regime})$$

For Al-Al₂O₃ junctions $w_p = \sqrt{\frac{\gamma}{C}} \sim 20 \text{ GHz}$
 $\gamma \sim C^{-1} \sim w_p \Rightarrow C \sim 5 \cdot 10^{-15} \text{ F}$ $\sim 1 \text{ K}$
 in the junction

The geometric capacitance is small if $l \ll 50 \mu\text{m}$


Adiabatic switch

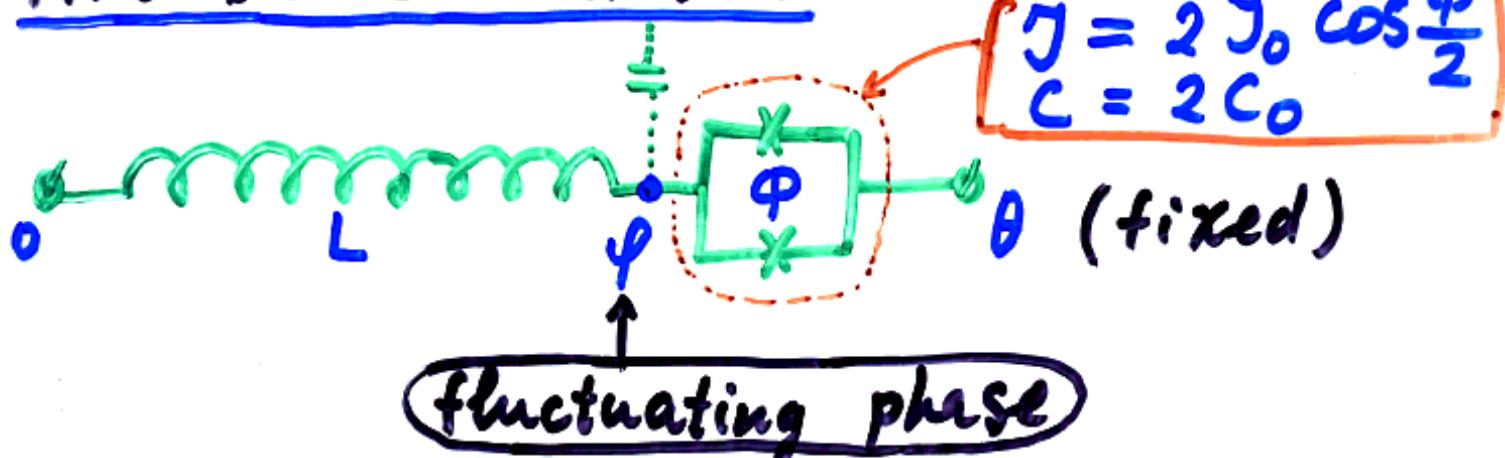

Superconducting current $I(\theta) = \frac{\partial E}{\partial \theta}$




I_{\max} change as a function of γ
by many orders of magnitude
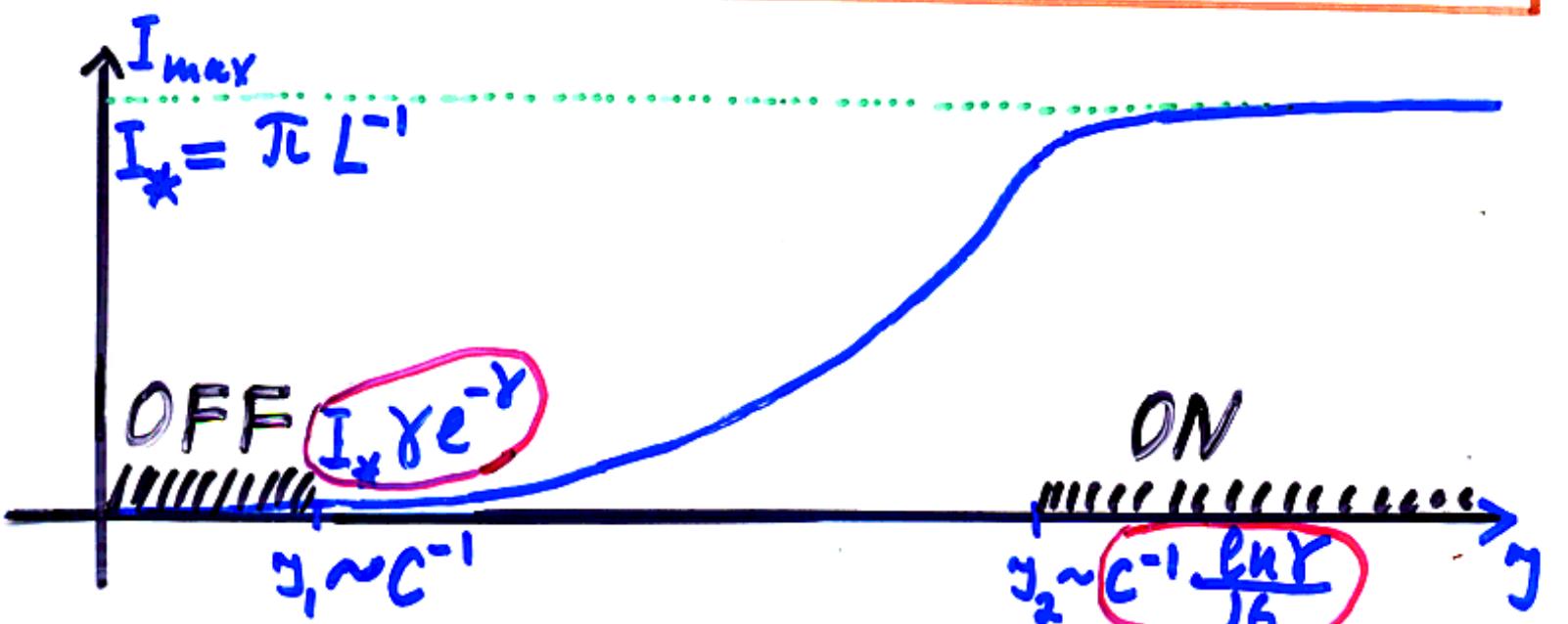
$$H = \frac{\varphi^2}{2L} - \gamma \cos(\varphi - \theta) + \frac{1}{2C} \left(i \frac{\partial \varphi}{\partial \theta} - n_g \right)^2$$




$$\gamma = \frac{1}{4} \sqrt{\frac{L}{C}}$$

Phase slips suppressed

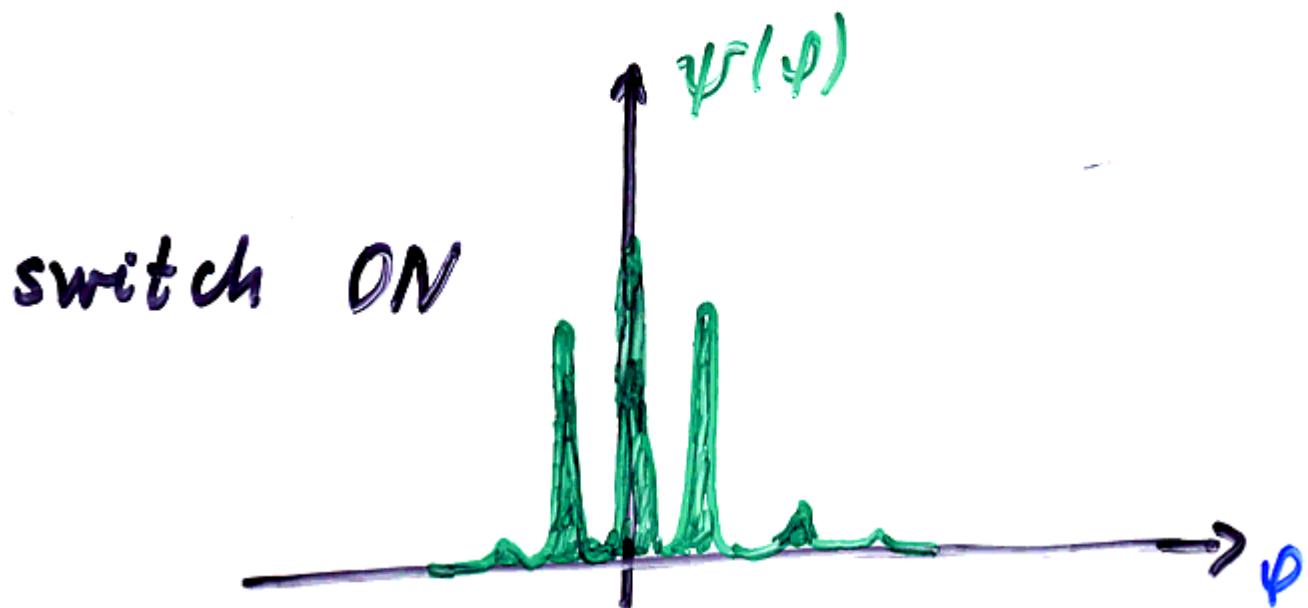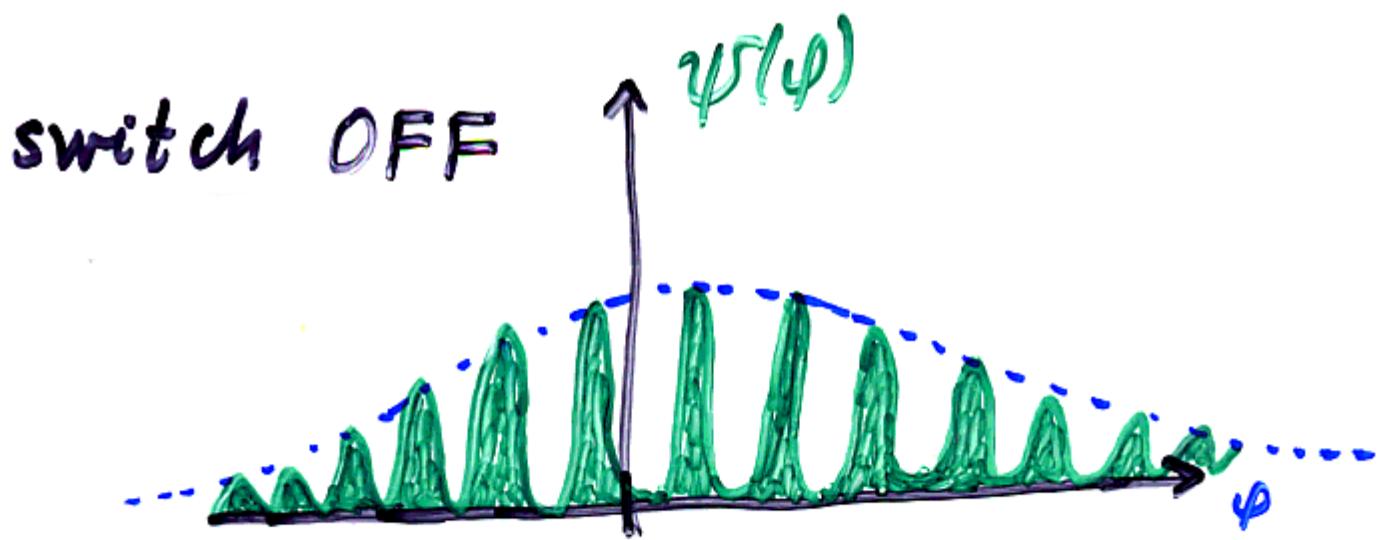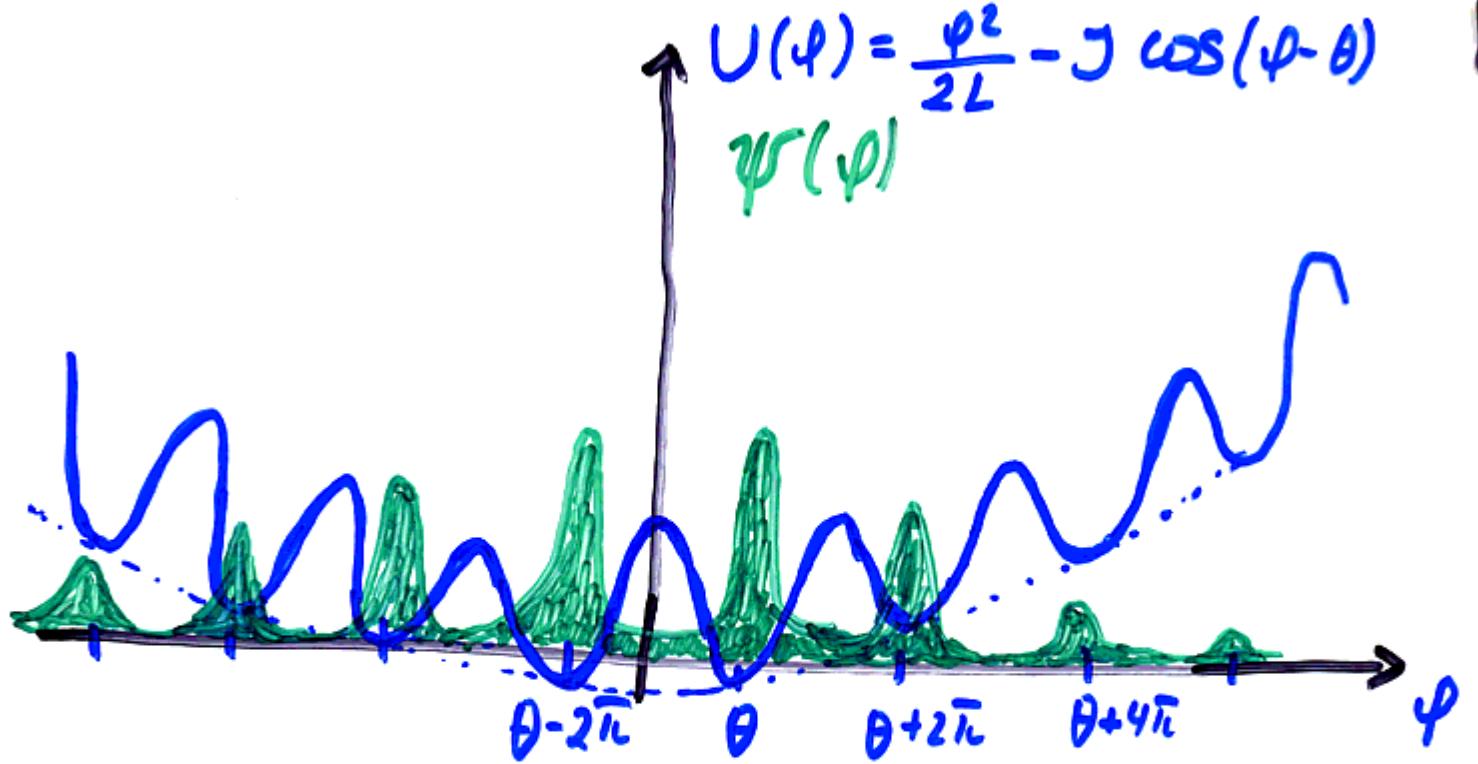

The physics is very simple:

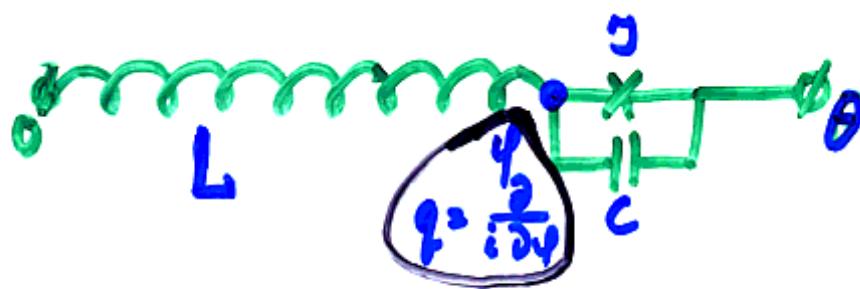


$$\psi \approx \theta + 2\pi n$$

1) If $L \rightarrow \infty$ then

$$H \approx -g \cos(\varphi - \theta) + \frac{1}{2C} \left(\frac{\partial}{\partial \varphi} - n_g \right)^2$$

φ varies from $-\infty$ to $+\infty$

Band structure:

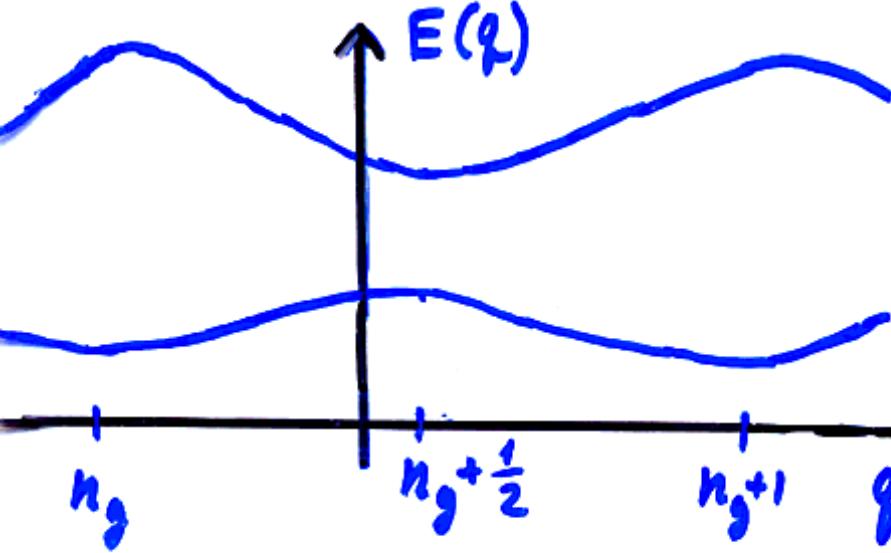

$$E = \frac{1}{C} f(\mu, q-h_g)$$


where $\mu = J C$,

If $\mu \gg 1$ then $f(\mu, q) \approx -t \cos(2\pi q)$

where $t \sim \sqrt{\mu} e^{-8\sqrt{\mu}}$ ← phase slip amplitude ($\times C$)

Switch is "closed" if $Ct \ll L^{-1}$

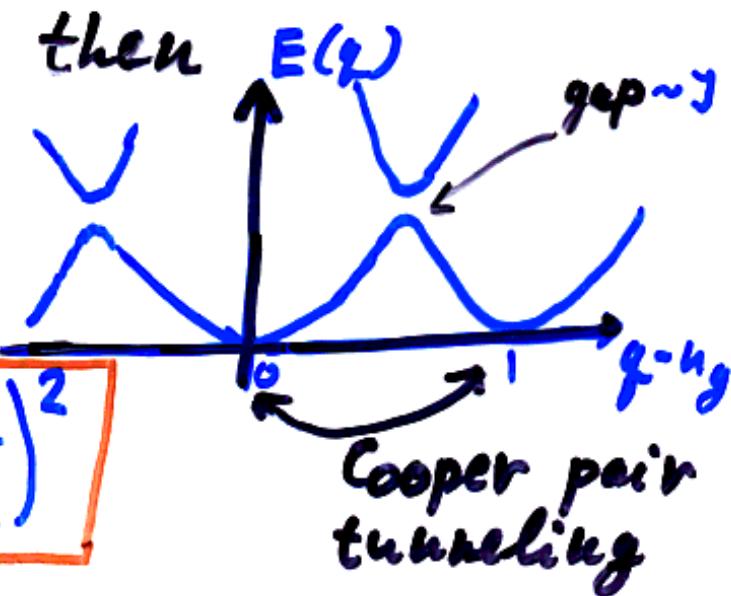2) If $M = JC \ll 1$
 $E(q) \approx \frac{(q - n_g)^2}{2C}$



$$H_{\text{eff}} = E(q) + \frac{1}{2L} \left(\frac{\partial}{i \partial q} \right)^2$$

Critical current $I_{\max} \sim$ tunneling amplitude

between $q = n_g$
 and $q = n_g + 1$


$$I_{\max} \sim L^{-1} \gamma e^{-\gamma}$$

$$\text{where } \gamma = \frac{1}{q} \sqrt{\frac{L}{C}}$$

Caveat : Large numeric factors may be involved.

DC transformer with 1:1 current ratio 11

(current mirror)

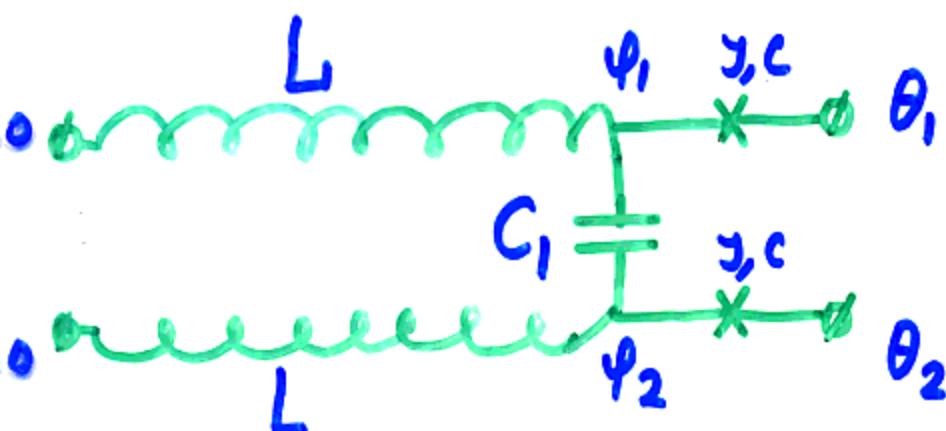

$$4\gamma C \sim 1$$

$$\gamma = \frac{1}{8} \sqrt{\frac{L}{C}} \gg 1$$

$$C_1 \gtrsim C \ln \gamma$$

$$H = \frac{\Phi_+^2}{L} + \frac{\Phi_-^2}{4L} + \frac{q_+^2}{4C} + \frac{q_-^2}{2C_1 + C} - 2\gamma \cos \frac{\Phi_- - \theta_1 + \theta_2}{2} x \\ \times \cos (\Phi_+ - \theta_1 - \theta_2)$$

where $\Phi_+ = \frac{\Phi_1 + \Phi_2}{2}$, $\Phi_- = \frac{\Phi_1 - \Phi_2}{2}$

fast slow

Equivalent circuits :


For Φ_+ :



$$I_{max} \sim L' \gamma e^{-\gamma}$$

(very small)

For Φ_- :

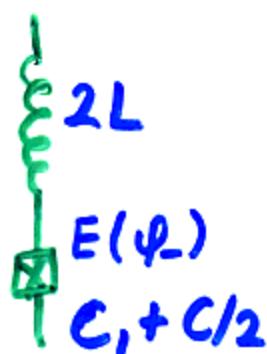


$$I_{max} \sim L^{-1}$$

(sufficiently large)

$$E(\theta_1, \theta_2) = \underbrace{F(\theta_1 - \theta_2)}_{\sim L^{-1} \gamma e^{-r}} + \underbrace{g(\theta_1, \theta_2)}_{\sim L^{-1} \gamma e^{-r}}$$

$$\min_n \frac{1}{4L} (\theta_1 - \theta_2 - 2\pi n)^2$$

More general situation:

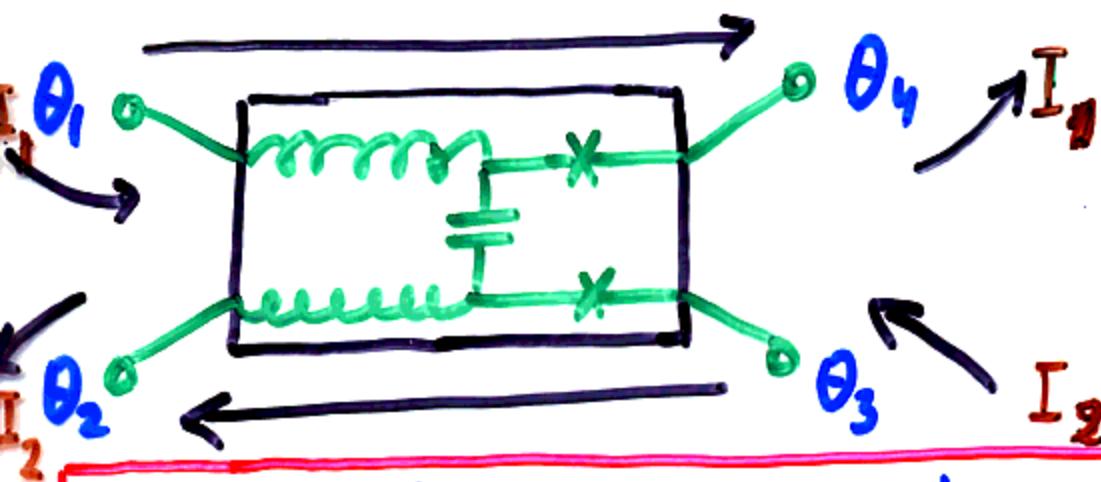


$$E = F(\theta_1 - \theta_2 + \theta_3 - \theta_4) + g(\theta_1, \theta_2, \theta_3, \theta_4)$$

$$I_1 \approx I_2 : \left\{ \begin{array}{l} I_1 - I_2 = \frac{\partial q}{\partial \theta_1} + \frac{\partial q}{\partial \theta_2} \sim L^{-1} \gamma e^{-r} \\ I_1 \approx I_2 < I_{\max} \approx \frac{\pi}{2L} \end{array} \right.$$

$$\text{No dissipation} \Rightarrow V_{14} \approx V_{23}$$

Turning a current mirror into a qubit

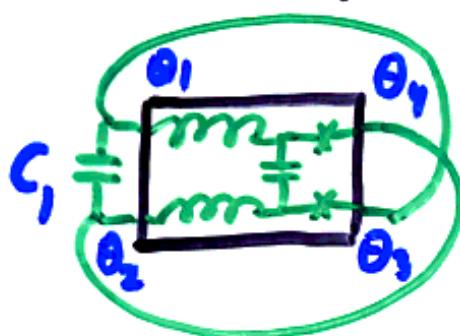


$$\Theta_1 = \Theta_3$$

$$\Theta_2 = \Theta_4$$

$$E = F(2(\theta_1 - \theta_2)) + h(\theta_1 - \theta_2)$$

exponentially suppressed

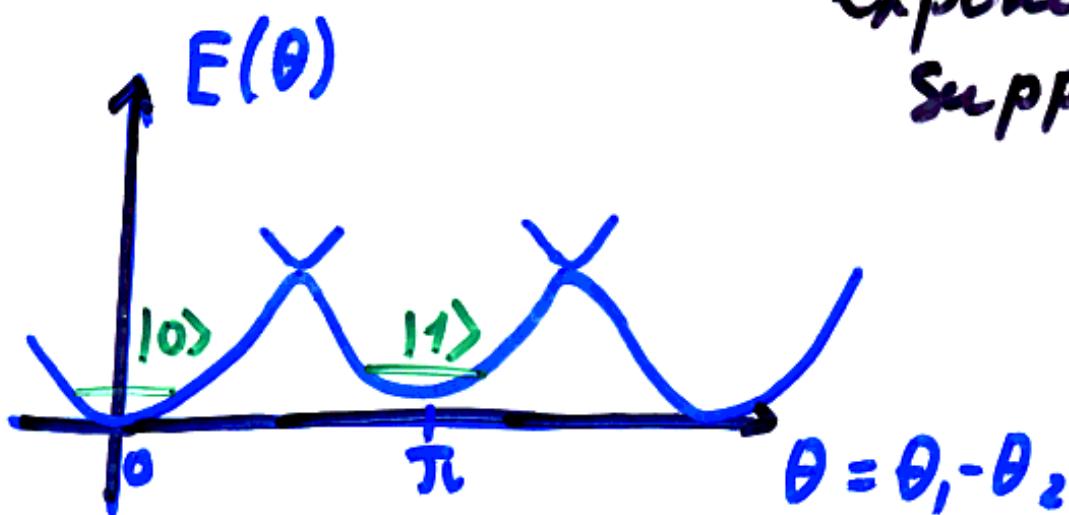

To prevent tunneling $|0\rangle \leftrightarrow |1\rangle$,


we need

$$JC_1 \gg 1$$

No phase slips in the inductors

Complete qubit

L14

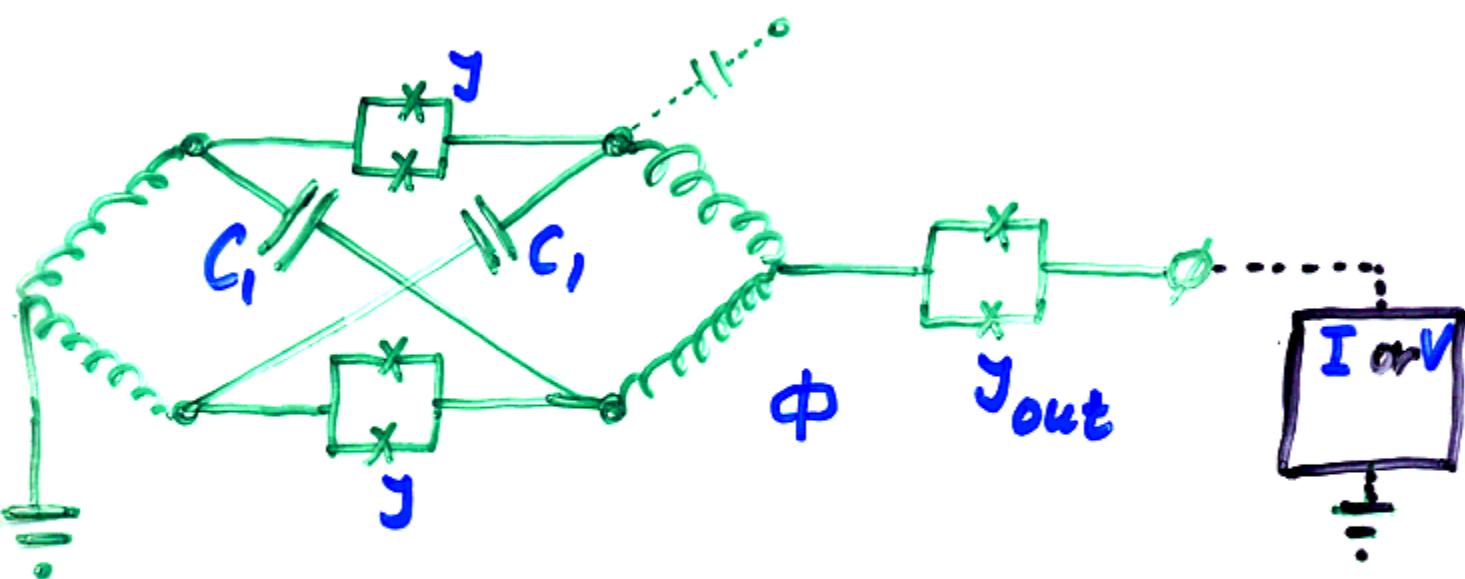

1) Quiet state:

J ON
J_{out} OFF

2) Phase measurement:

$|0\rangle$ vs $|1\rangle$

$$I_{\text{out}} \sim \frac{1}{L}$$

J ON
J_{out} ON

3) Dual measurement

$$\frac{|0\rangle + |1\rangle}{\sqrt{2}} \quad \text{vs} \quad \frac{|0\rangle - |1\rangle}{\sqrt{2}}$$

J OFF
J_{out} OFF

$$V_{\text{out}} \sim \frac{1}{C_1}$$